

**On the Improved Implementations and Performance  
Evaluation of Digit-by-Digit Integer Restoring  
and Non-Restoring Cube Root Algorithms**

Yamin Li

Dept. of Computer Science

Hosei University

<http://cis.k.hosei.ac.jp/~yamin/>

# Cube Root Algorithms and Implementations

- Algorithms
  - Digit-by-digit integer restoring
  - Digit-by-digit integer non-restoring
- Improved implementations
  - Basic implementations
  - Eliminating multiplications
  - Calculating  $12q^2$  in advance
  - Using carry save adders (CSAs)
- Cost / performance evaluation



# Cube Root

- Given a radicand  $d$ , calculate the cube root  $q$  so that

$$d = q^3 + r$$


- Ex.  $26 = 2^3 + 18$  (We consider only  $d \geq 0$ )
- Assume that  $d$  has 33 bits. Then
  - $q$  has 11 bits (33/3 bits)
  - $r$  has 24 bits at most
    - $d = q^3 + r < (q + 1)^3 = q^3 + 3q^2 + 3q + 1$
    - $\Rightarrow r \leq 3q^2 + 3q \Rightarrow 2 + 11 \times 2$  bits
    - In order to check the sign of the partial remainder, we use 25 bits during the calculation

# Definition of Partial Cube Root $q_i$

  

Register `reg_q` stores cube root
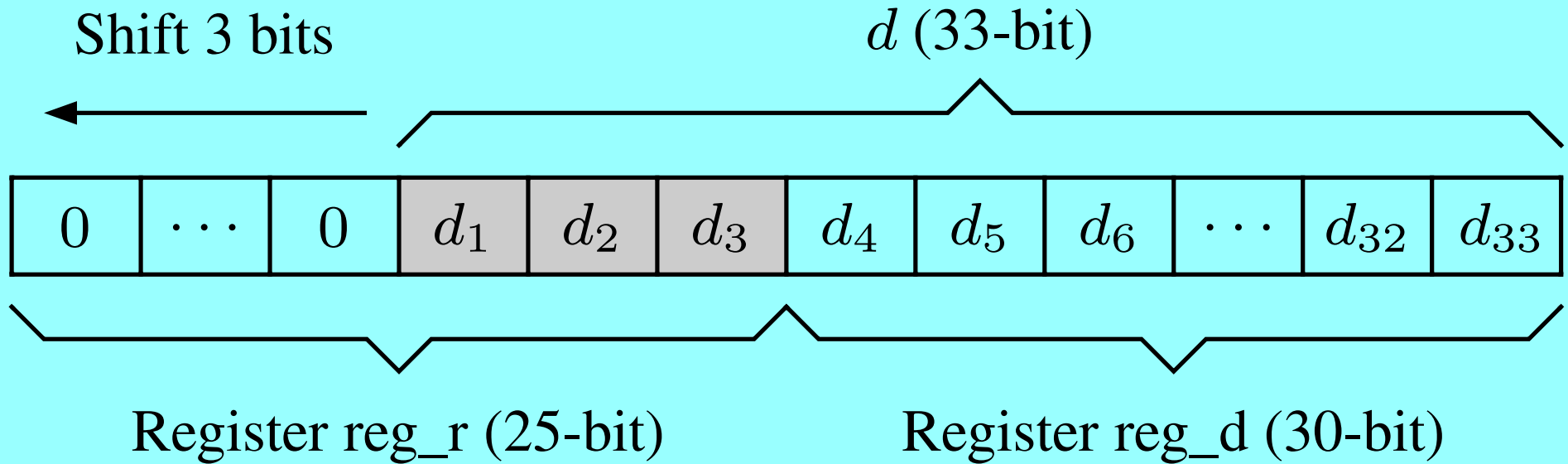
# Initial Values of Registers `reg_r` and `reg_d`



Register `reg_r` stores remainder

Register `reg_d` stores radicand

# Basic Restoring Cube Root Algorithm

- Radicand  $d = \{d_1, d_2, d_3, \dots, d_{33}\} = q^3 + r$
- Suppose that we have got a partial cube root  $q_i$  and a partial remainder  $r_i$  such that the partial radicand

$$\{d_1, d_2, \dots, d_{3i}\} = q_i^3 + r_i$$

- To calculate  $b_{i+1}$  and  $r_{i+1}$ , we have

$$\{d_1, d_2, \dots, d_{3i}, d_{3i+1}, d_{3i+2}, d_{3i+3}\} = q_{i+1}^3 + r_{i+1}$$

where  $q_{i+1} = \{q_i, b_{i+1}\}$  or  $q_{i+1} = 2q_i + b_{i+1}$

# Basic Restoring Cube Root Algorithm

■ Let  $p_i = \{d_{3i+1}, d_{3i+2}, d_{3i+3}\}$ , then

$$\begin{aligned}r_{i+1} &= \{d_1, d_2, \dots, d_{3i}, p_i\} - q_{i+1}^3 \\ &= 8(\{d_1, d_2, \dots, d_{3i}\}) + p_i - q_{i+1}^3 \\ &= 8(q_i^3 + r_i) + p_i - (2q_i + b_{i+1})^3 \\ &= 8r_i + p_i - (12q_i^2 b_{i+1} + 6q_i b_{i+1}^2 + b_{i+1}^3) \\ &= \{r_i, p_i\} - (12q_i^2 b_{i+1} + 6q_i b_{i+1}^2 + b_{i+1}^3)\end{aligned}$$

■ Assume  $b_{i+1} = 1$

$$r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1)$$

# Basic Restoring Cube Root Algorithm

- $r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1)$

- If  $r_{i+1} \geq 0$ , then  $b_{i+1} = 1$ ,

$$q_{i+1} = \{q_i, 1\}$$

- Otherwise,  $b_{i+1} = 0$ ,


$$q_{i+1} = \{q_i, 0\}$$

and we restore  $r_{i+1}$  by adding  $(12q_i^2 + 6q_i + 1)$  to the negative remainder



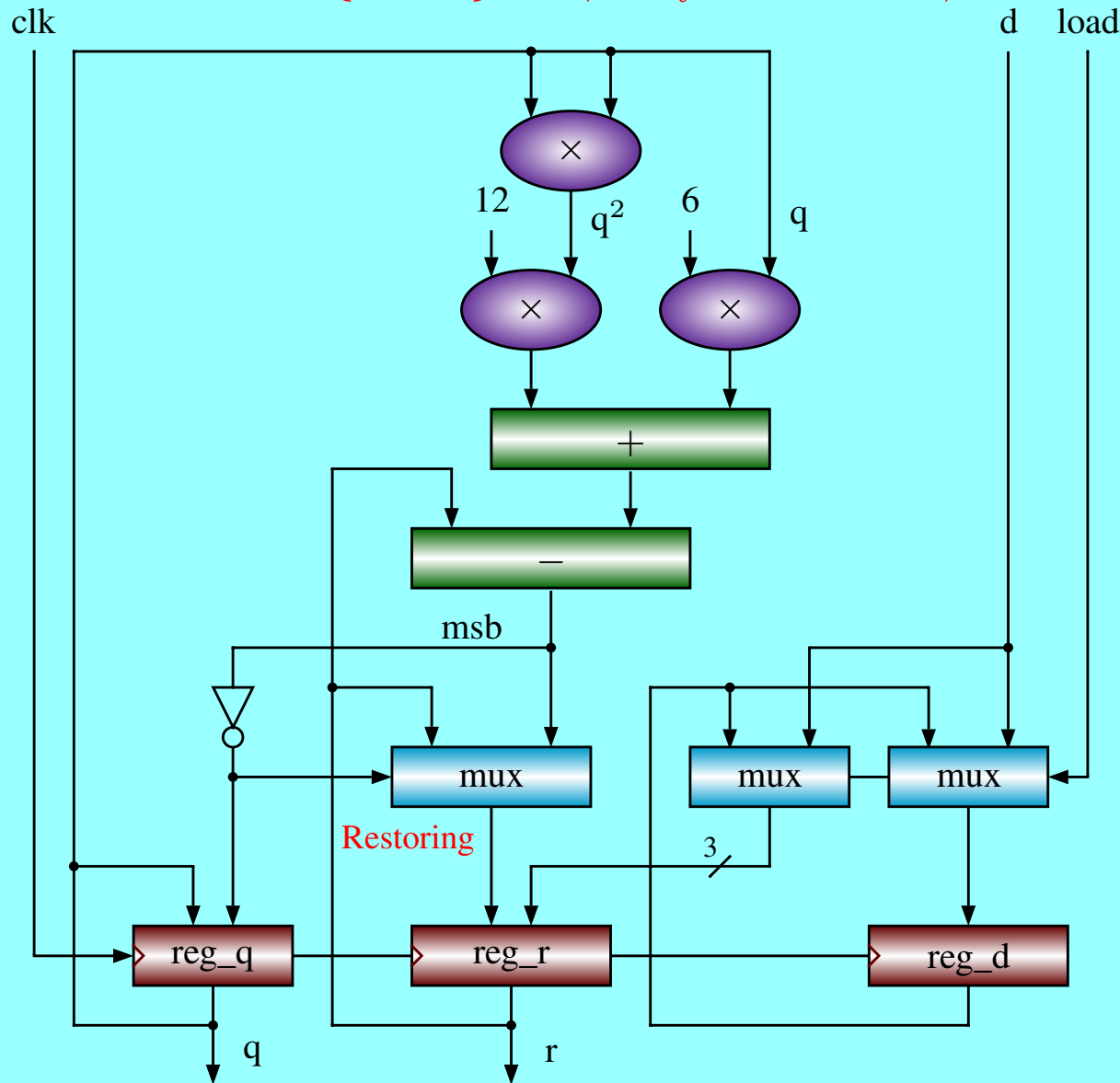
# Circuit of Restoring Cube Root (Using mul)

$$r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1)$$


 
# Waveform of Restoring Cube Root Algorithm



- Implemented on Altera Cyclone IV E EP4CE115F29C7
- 160 LEs (logic elements)
- 72 DFFs (D flip-flops)
- Two embedded multiplier 9-bit elements
- Maximum clock frequency: **73.87 MHz**

# Eliminating Multiplications

■ Let  $s_i = q_i^2$

■ For the case of  $b_{i+1} = 0$

$$s_{i+1} = q_{i+1}^2 = (2q_i + 0)^2 = 4q_i^2 = 4s_i$$

■ For the case of  $b_{i+1} = 1$


$$s_{i+1} = q_{i+1}^2 = (2q_i + 1)^2 = 4q_i^2 + 4q_i + 1 = 4s_i + 4q_i + 1$$

■ Then  $r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1)$  became


$$r_{i+1} = (\{r_i, p_i\} - (8s_i + 4s_i)) - (4q_i + 2q_i + 1)$$
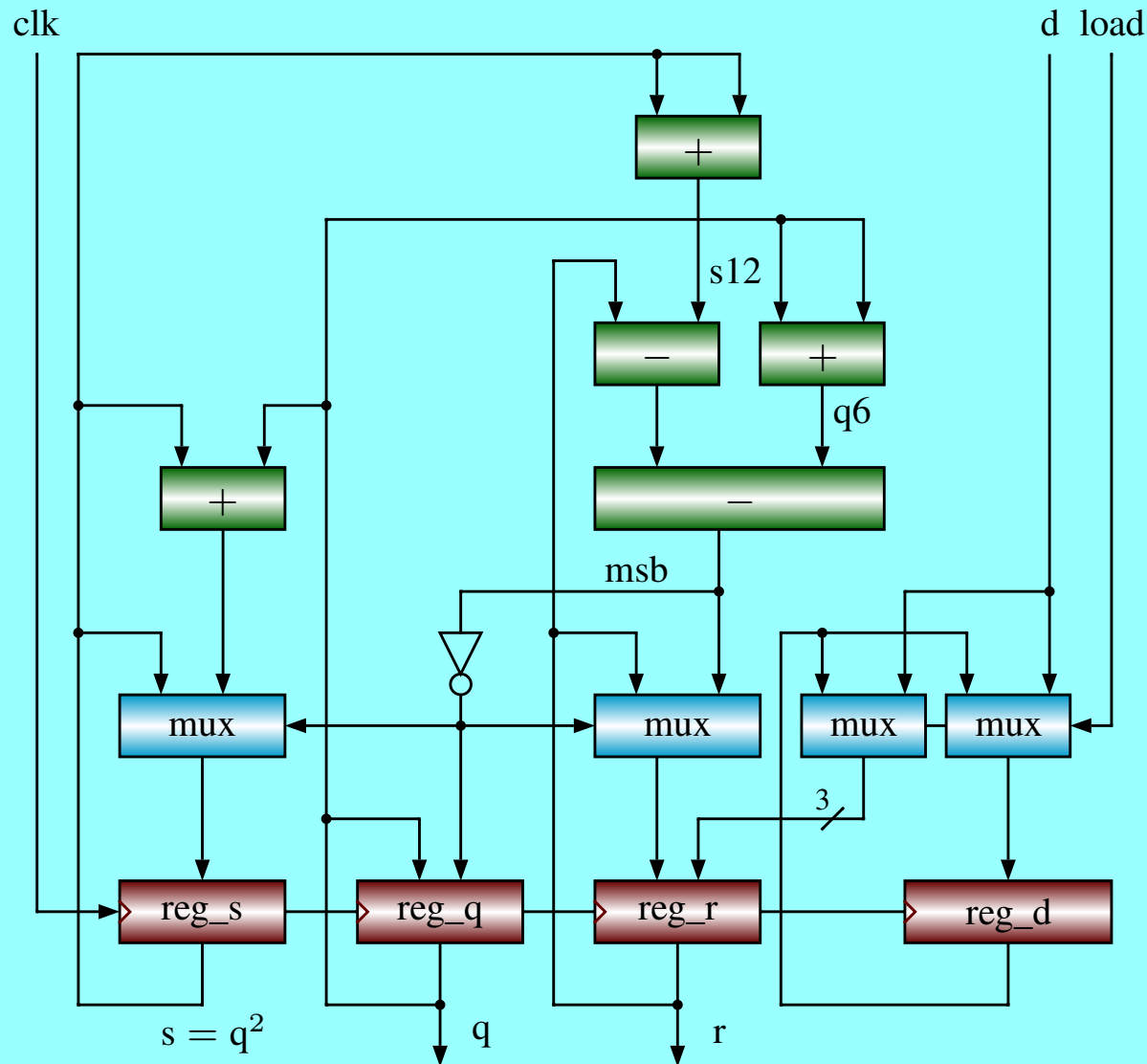
# Circuit of Restoring Cube Root (No mul)

$$r_{i+1} = (\{r_i, p_i\} - (8s_i + 4s_i)) - (4q_i + 2q_i + 1)$$


 
# Waveform of Restoring Cube Root Algorithm



- Implemented on Altera Cyclone IV E EP4CE115F29C7
- 220 LEs (logic elements) (160)
- 92 DFFs (D flip-flops) (72)
- No embedded multiplier is required (2)
- Maximum clock frequency: **126.06 MHz** (73.87 MHz)

# Calculating $12q^2$ in Advance

■ Let  $w_{i+1} = 12s_{i+1}$

■ For the case of  $b_{i+1} = 0$

$$w_{i+1} = 12q_{i+1}^2 = 12(2q_i + 0)^2 = 48s_i$$

■ For the case of  $b_{i+1} = 1$

$$w_{i+1} = 12q_{i+1}^2 = 12(2q_i + 1)^2 = 48s_i + 48q_i + 12$$

■ Then the calculation of  $r_{i+1}$  became

$$r_{i+1} = (\{r_i, p_i\} - w_i) - (4q_i + 2q_i + 1)$$

# Algorithm 1: cube\_root\_restoring ( $d, q, r$ )

**Input:** 33-bit radicand  $d = \{d_1, d_2, \dots, d_{33}\}$


**Output:** 11-bit cube root  $q = \{b_1, b_2, \dots, b_{11}\}$

**Output:** 24-bit remainder  $r$

```
begin
   $r \leftarrow \{0, \dots, 0, d_1, d_2, d_3\};$  /* 25 bits */
   $d \leftarrow \{d_4, \dots, d_{33}\};$  /* 30 bits */
   $q \leftarrow \{0, \dots, 0\};$  /* 11 bits */
   $s \leftarrow \{0, \dots, 0\};$  /*  $s = q^2$ , 22 bits */
   $w \leftarrow \{0, \dots, 0\};$  /*  $w = 12q^2$ , 25 bits */
  for  $i \leftarrow 1$  to 11 do
     $p = d[29 : 27];$  /* 3 leftmost bits of  $d$  */
     $t = (r - w) - (\{q, 0, 1\} + \{q, 0\});$  /* rem */
    if ( $t \geq 0$ ) /* rem is non-negative */
       $w \leftarrow (\{s, 0, 0, 0, 0, 0\} + \{q, 0, 1, 0, 0, 0\}) +$ 
         $(\{s, 0, 0, 0, 0, 0\} + \{q, 0, 1, 0, 0\});$ 
       $s \leftarrow \{s, 0, 0\} + \{q, 0, 1\};$  /*  $\{q, 1\}^2$  */
       $q \leftarrow \{q, 1\};$  /*  $b_i = 1$  */
      if ( $i < 11$ )  $r \leftarrow \{t, p\};$  /* new  $r$  */
      else  $r \leftarrow t[23 : 0];$  /* final  $r$  */
      endif
    else /* rem is negative */
       $w \leftarrow \{s, 0, 0, 0, 0, 0\} + \{s, 0, 0, 0, 0\};$ 
       $s \leftarrow \{s, 0, 0\};$  /*  $\{q, 0\}^2$  */
       $q \leftarrow \{q, 0\};$  /*  $b_i = 0$  */
      if ( $i < 11$ )  $r \leftarrow \{r, p\};$  /* restoring  $r$  */
      else  $r \leftarrow r[23 : 0];$  /* final  $r$  */
      endif
    endif
     $d \leftarrow \{d, 0, 0, 0\};$  /* shift 3-bit left */
  endfor
end
```
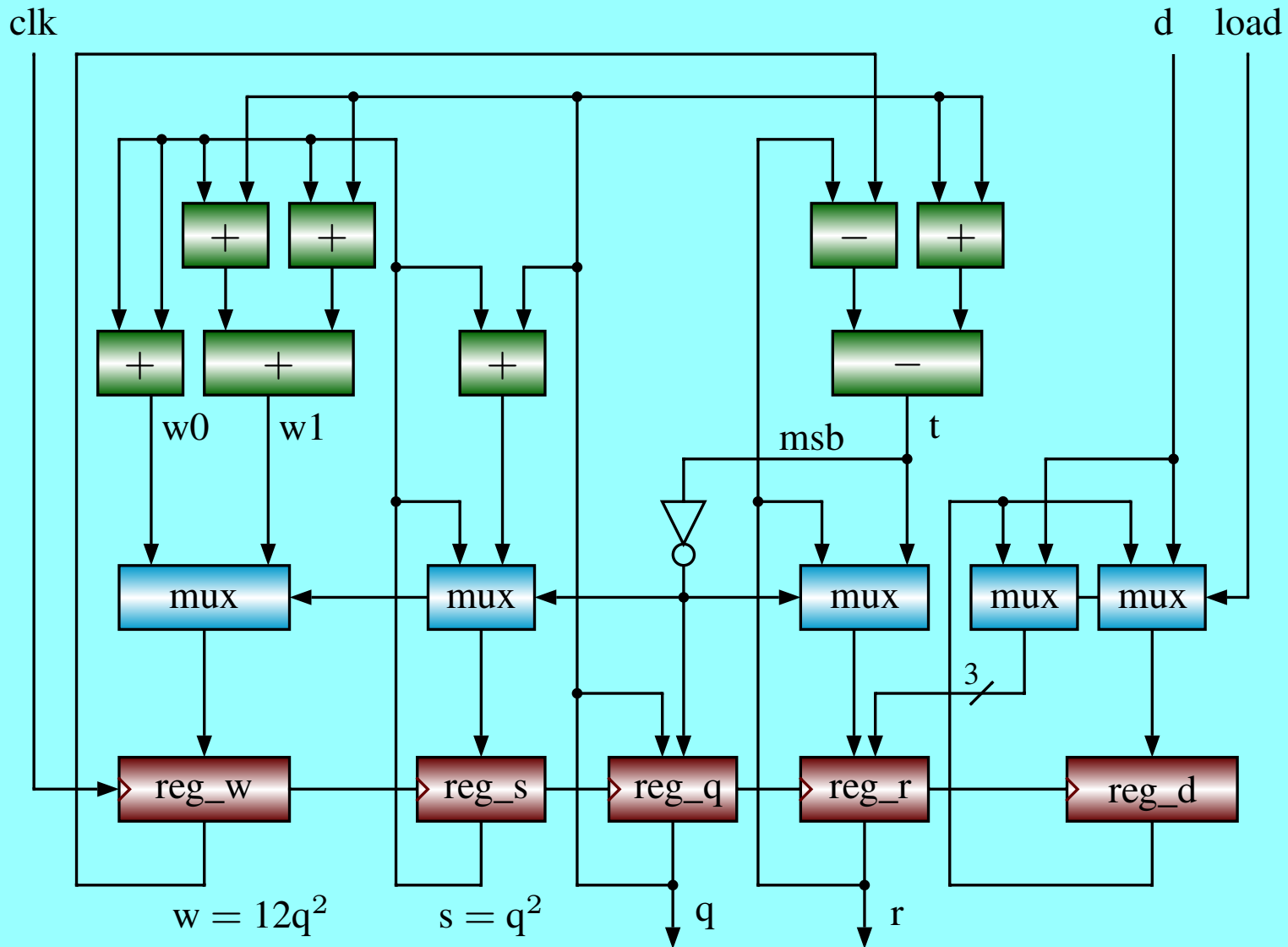
# Circuit of Restoring Cube Root (Balanced)

$$r_{i+1} = (\{r_i, p_i\} - w_i) - (4q_i + 2q_i + 1)$$





# cube\_root\_restoring.v

```
// Copyright by Yamin Li and Wanming Chu, 2016
module cube_root_restoring (
    input  [32:0] d,           // 33-bit radicand
    input          load,      // start
    input          clk,       // clock
    input          clrn,      // reset
    output [10:0] q,          // 11-bit cube root
    output [23:0] r,          // 24-bit remainder
    output reg     busy,     // circuit busy
    output reg     ready);   // results ready

    reg  [29:0] reg_d;        // register for d
    reg  [10:0] reg_q;        // register for q
    reg  [24:0] reg_r;        // register for r
    reg  [23:0] reg_w;        // register for  $12q^2$ 
    reg  [21:0] reg_s;        // register for  $q^2$ 
    reg   [3:0] count;        // counter for control
    wire [24:0] rem;         // signed remainder
```

# cube\_root\_restoring.v

```
wire    [23:0] w0,w1,w;           // for reg_w
wire    [21:0] rs;                // for reg_s
wire    [24:0] rr;                // for reg_r
assign  w0    =  {reg_s[18:0],5'd0} +           // 32q^2
                 {reg_s[19:0],4'd0};          // 16q^2
assign  w1    =  ({reg_s[18:0],5'd0} +           // 32q^2
                 { 8'd0,reg_q,5'd8})+         // 32q+8
                 ({reg_s[19:0],4'd0} +           // 16q^2
                 { 9'd0,reg_q,4'd4});          // 16q+4
assign  rem   =  (reg_r - {1'd0,reg_w}) -       // r-w
                 ({12'd0,reg_q,2'd0} +         // 4q
                 {13'd0,reg_q,1'd1});          // 2q+1
wire    b     =  ~rem[24];           // root bit
assign  rs    =  b ? {reg_s[19:0],2'd0} +       // 4q^2
                 { 9'd0,reg_q,2'd1} :         // 4q+1
                 {reg_s[19:0],2'd0};          // 4q^2
assign  rr    =  b ? {  rem[21:0],reg_d[29:27]} :
                 {reg_r[21:0],reg_d[29:27]};
```


# cube\_root\_restoring.v

```
assign w      = b ? w1 : w0;                //  $12q^2$ 
wire  [3:0] count_plus = count + 4'd1;
wire          counter10 = (count == 4'd10);
always @ ( posedge clk or negedge clrn ) begin
    if (!clrn) begin                        // on reset, active low
        busy  <= 0;                          // circuit is not busy
        ready <= 0;                          // results are not ready
    end else begin                          // not on reset
        if (load) begin                    // load radicand d
            reg_d <= d[29:0];                // 30 bits
            reg_q <= 0;                      //  $q_0=0$ 
            reg_r <= {22'd0, d[32:30]};      //  $r_0$ 
            reg_s <= 0;                      //  $q^2$ 
            reg_w <= 0;                      //  $12q^2$ 
            busy  <= 1;                      // circuit is busy
            ready <= 0;                      // results are not ready
            count <= 0;                      // clear counter
        end else if (busy) begin           // calculating
```

# cube\_root\_restoring.v

```
    reg_d <= {reg_d[26:0], 3'd0};           // shift
    reg_q <= {reg_q[9:0], b};             // shift
    reg_s <= rs;                          // q^2
    reg_w <= w;                            // 12q^2
    if (counter10) begin                  // finish
        busy <= 0;                        // circuit is idle
        ready <= 1;                       // results are ready
        if (b) reg_r <= rem;              // remainder
    end else begin                        // not finish
        reg_r <= rr;
    end
    count <= count_plus;                  // counter++
end
end
end
assign q = reg_q;                        // final cube root
assign r = reg_r[23:0];                  // final remainder
endmodule
```
 
# Waveform of Restoring Cube Root Algorithm



- Implemented on Altera Cyclone IV E EP4CE115F29C7
- 271 LEs (logic elements) (220)
- 109 DFFs (D flip-flops) (92)
- No embedded multiplier is required (0)
- Maximum clock frequency: **134.44 MHz** (126.06 MHz)

# Using Carry Save Adders


- Two-level carry propagate adders (CPAs) to calculate  $t$
- We can use the carry save adders (CSAs) to speed up it

$$\begin{aligned}t &= \{r, p\} - w - 4q - 2q - 1 \\ &= \{r, p\} + (\overline{w} + 1) + (\overline{4q} + 1) + (\overline{2q} + 1) - 1 \\ &= \{r, p\} + \overline{w} + \overline{4q} + \overline{2q} + 1 + 1\end{aligned}$$


- We use two-level CSAs to perform the additions and get two numbers: carry  $c$  and sum  $s$
- Then we use a CPA to get the temporary remainder

$$t = 2c + s$$

# Using Carry Save Adders

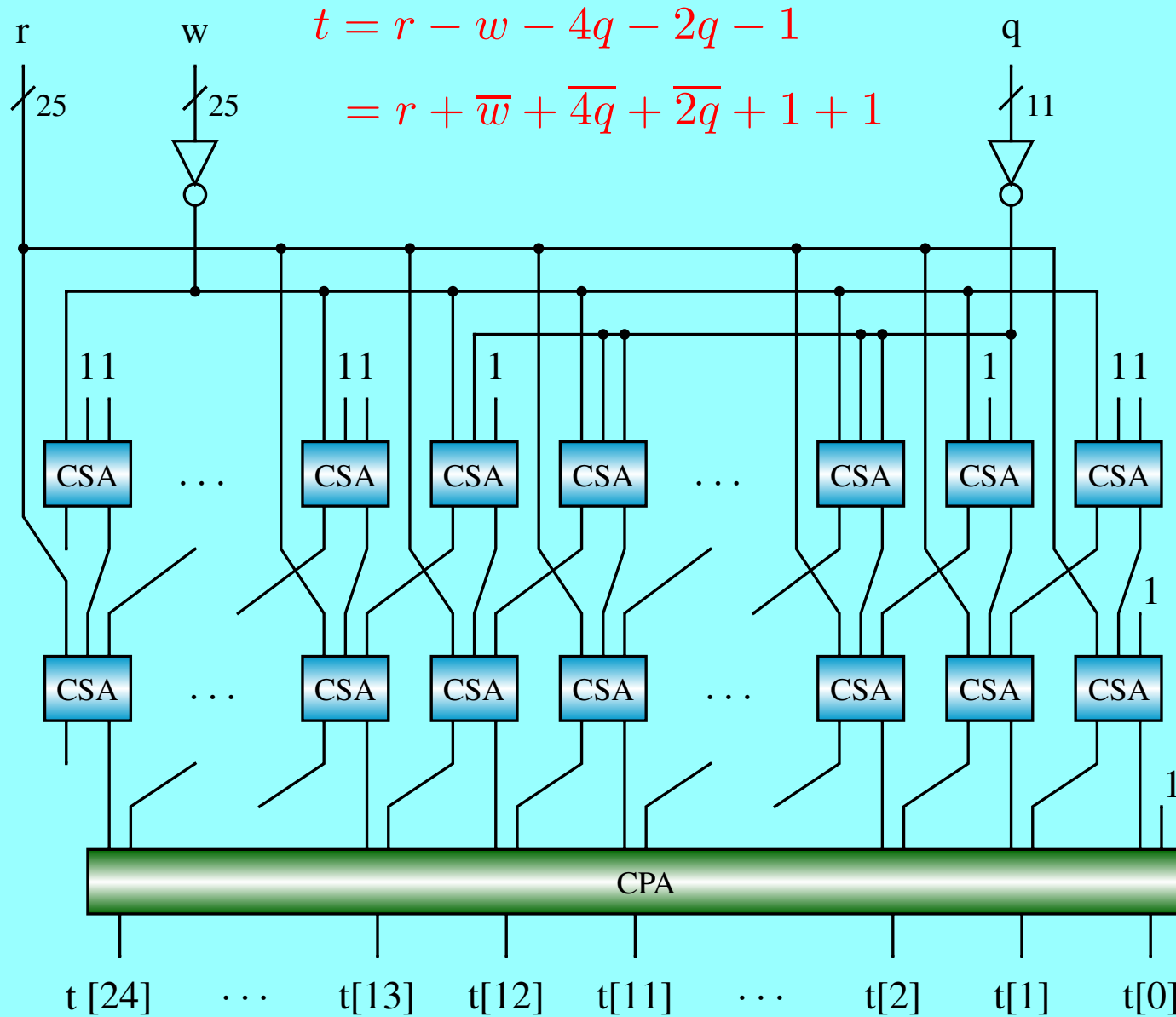
 
# Waveform of Restoring Cube Root Algorithm



- Implemented on Altera Cyclone IV E EP4CE115F29C7
- 298 LEs (logic elements) (271)
- 109 DFFs (D flip-flops) (109)
- No embedded multiplier is required (0)
- Maximum clock frequency: **147.47 MHz** (134.44 MHz)



# Non-Restoring Cube Root Algorithms

- In restoring algorithm, if  $r_i < 0$ ,  $r_i$  is restored by adding  $(12q_{i-1}^2 + 6q_{i-1} + 1)$  to  $r_i$
- Then we perform  $r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1)$
- Because  $q_i = \{q_{i-1}, 0\}$  or  $q_{i-1} = q_i/2$ , we have

$$\begin{aligned}r_{i+1} &= (8(r_i + 12q_{i-1}^2 + 6q_{i-1} + 1) + p_i) - (12q_i^2 + 6q_i + 1) \\ &= (8r_i + 24q_i^2 + 24q_i + 8 + p_i) - (12q_i^2 + 6q_i + 1) \\ &= \{r_i, p_i\} + 12q_i^2 + 18q_i + 7\end{aligned}$$

- Non-restoring cube root algorithm


$$r_{i+1} = \{r_i, p_i\} - (12q_i^2 + 6q_i + 1) \text{ if } r_i \geq 0$$

$$r_{i+1} = \{r_i, p_i\} + (12q_i^2 + 18q_i + 7) \text{ if } r_i < 0$$

# Cost / Performance Evaluation

Implementation	Frequency	Cycle time	Latency	Logic	Reg	Mul
1. Restoring (Mul)	73.87 MHz	13.54 ns	148.91 ns	160	72	2
2. Restoring (NoMul)	126.06 MHz	7.93 ns	87.26 ns	220	92	0
3. Restoring (Advance)	134.44 MHz	7.44 ns	81.82 ns	271	109	0
4. Restoring (CSAs)	147.47 MHz	6.78 ns	74.59 ns	298	109	0
5. Non-rest. (Mul)	77.77 MHz	12.86 ns	141.44 ns	338	73	2
6. Non-rest. (NoMul)	115.23 MHz	8.68 ns	95.46 ns	380	93	0
7. Non-rest. (Advance)	122.03 MHz	8.19 ns	90.14 ns	433	112	0
8. Non-rest. (CSAs)	137.70 MHz	7.26 ns	79.88 ns	492	112	0

# Cost / Performance Evaluation

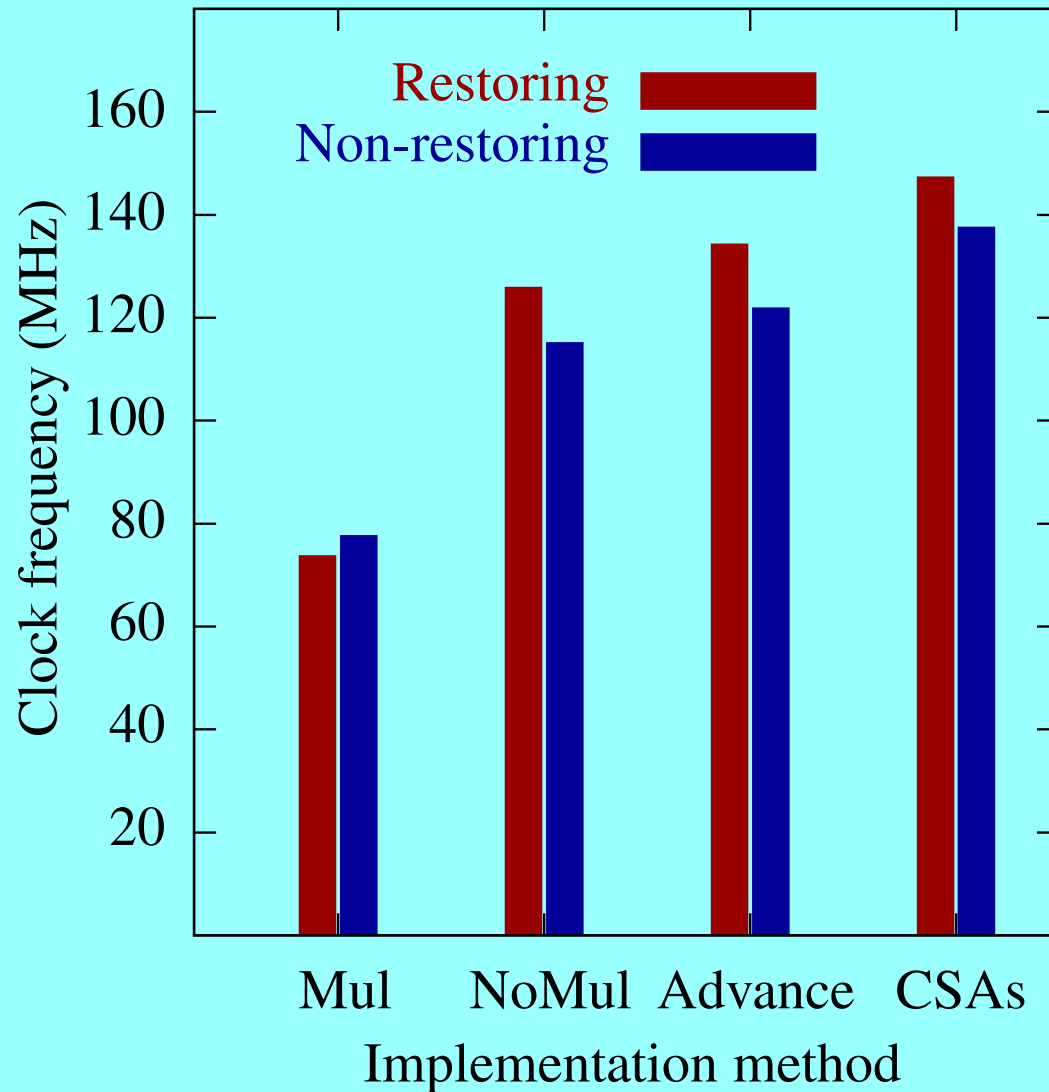

Restoring cube root:

$$\text{Speedup}_{CSA} =$$

$$147.47 / 73.87 = 199.63\%$$

Non-restoring cube root:

$$\text{Speedup}_{CSA} =$$

$$137.70 / 77.77 = 177.06\%$$

Both are low at cost

# FYI: Square Root Algorithms

---

- Square Root Algorithms

- Restoring and non-restoring algorithms

- Goldschmidt algorithm

- Newton-Raphson algorithm

- Refer to

- Yamin Li, “Computer Principles and Design in Verilog HDL”, *John Wiley & Sons*, ISBN 978-1-118-84109-9, 2015, 550 pages

- Thank you very much!